

INSTRUMENTS

Measure Resistances with Six Wires

Martin Rowe
Senior Technical Editor

To measure the value of a single resistor that's not installed in a circuit, you just connect the resistor to a DMM and measure the resistance. But what if you can't separate the resistor from its circuit? That's the problem manufacturers of resistor networks, sensors, and connectors face. Line-termination networks, for example, have resistors in parallel that combine to produce wrong measurements.

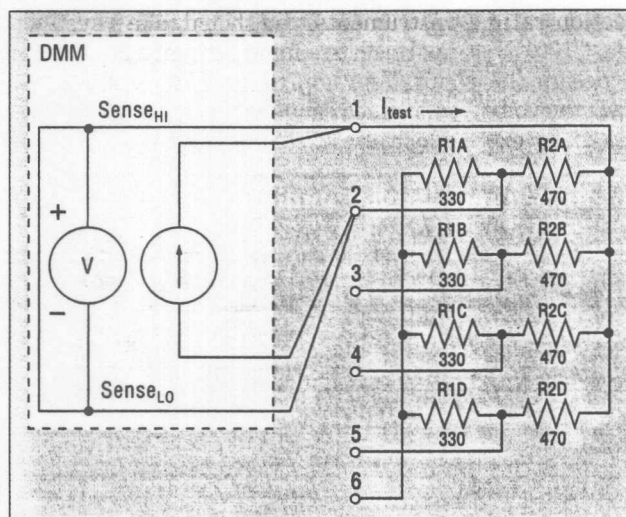


FIGURE 1 The DMM can't measure R_{2A} unless you remove the resistor from the circuit.

In some circuits, resistors are connected across protection diodes, which also alter measurements.

If you're trying to measure the resistance in a section of a PCB trace, you may find a trace that has other traces connected to it. To measure resistance, you have two choices: You can cut the trace and connect your DMM to the resistor, or you can use the six-wire method, called "guarding," to isolate the unknown resistance from the rest of the circuit. The six-wire method requires at least two series resistors in parallel with the unknown resistance.

In **Figure 1**, you can't use a four-wire DMM to measure the value of R_{2A} without disconnecting the resistor from the network. If you connect a DMM's source and sense leads to pins 1 and 2 of the resistor network, you'll measure R_{2A} in parallel with three sets of resistors, which calculates to $597\ \Omega$ in parallel with R_{2A} . That's an equivalent resistance of $262\ \Omega$. If you could force the current in R_{1A} to zero, however, then all of I_{test} could flow through R_{2A} and no current would flow through the other resistors (R_{1B} to R_{2D}). You'd get the correct reading.

Six from Four

Figure 2 shows that adding an op amp and two wires to a four-wire resistance measurement produces a six-wire measurement. Resistor R_{2A} is the resistor under test. R_{eq} represents the equivalent value of the parallel resistor pairs in the network— R_{1B} through R_{2D} in **Figure 1** ($597\ \Omega$). The op amp, configured as a voltage follower, forces the voltage

across R_{eq} to nearly zero. Therefore, most of I_{test} should flow through R_{2A} .

A simple and elegant solution? Well, almost. No op amp is perfect, so it can always introduce errors. Manufacturers of DMMs with six-wire ohms measurement capabilities have to add circuits to compensate for those errors.

The op amp's offset voltage, V_{OS} , contributes to measurement errors. That voltage, typically in microvolts, will cause some current to flow through R_{2A} , which affects I_{test} .

Assume that each " R_1 " resistor in the network is $330\ \Omega$ nominal and each " R_2 " resistor is $470\ \Omega$ nominal. The value of

World Class Safety Analyzer

NEW




Entry Level Price!

Getting an automated multi-function electrical safety analyzer used to mean spending big money. Not anymore. For about the price of a semi-automated Hipot tester, you can now get the top quality, fully automated Vitrek V Series. The Safety Analyzers that deliver uncompromised performance and functionality with the features you need to get the job done right.

The Intelligent Hipot Advantage

- High Speed Operation
- GPIB, RS232, PLC & Print Out
- 100 Test Sequence Storage
- Up to 35mA source, 1nA sense
- 1 Touch user interface
- Selectable Arc Detection
- AC, DC, IR & 30A Ground Bond
- Available 48 Point Scanner

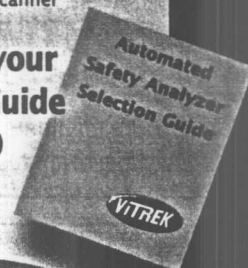Call now for your
FREE Safety Guide
858.558.4530



World Leaders in Compliance Automation

US Corporate Headquarters
Voice: 858.558.4530 Fax: 858.558.9688
www.vitrekt.com
e-mail: info@vitrek.com

*US List Price.
© Vitrek Corporation 2000.
All rights reserved. TMW2/00

ENTER 14 AT TMWORLD.COM/TIX

R_{eq} is $(330+470)/3$ or $267\ \Omega$. If V_{OS} is $20\ \mu\text{V}$ and I_{test} is $1\ \text{mA}$, then the error caused by V_{OS} and R_{eq} is: $\text{Error} (\%) = (V_{OS}/(R_{eq} * I_{test})) * 100$, which is 0.0075% .

A 0.0075% error doesn't seem like much, but if you're measuring the resistance of a PCB trace, then R_A can reduce to less than $1\ \Omega$, which increases the error significantly. As R_A approaches zero, the error it contributes approaches infinity. So, you can't use the six-wire method to measure a resistance unless the unknown resistor has at least two series resistances in parallel with it.

The op amp must also supply enough current through $R1A$ so the voltage across $R1A$ equals the voltage across $R2A$. To further reduce errors, the DMM manufacturers will automatically adjust V_{OS} closer to $0\ \text{V}$.

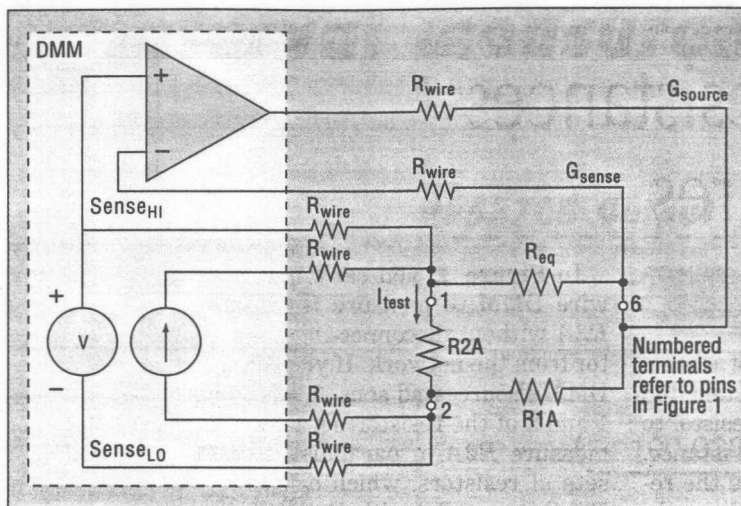


FIGURE 2 The op-amp forces little or no current to flow through R_{eq} so all of I_{test} flows through $R2A$.


Common-mode voltages contribute to measurement errors, too. Meter designers prefer op amps with as high a common-mode rejection ratio (CMRR) as possible—at least $100\ \text{dB}$.

Manufacturers may also design the op amp's power supply to track the voltage at the Sense_{HI} connection. If, for ex-

ample, the voltage at Sense_{HI} is $5\ \text{V}$ and the op amp's power supply covers a range of $30\ \text{V}$, then the meter will adjust the op amp's power supply to $+20\ \text{V}$ and $-10\ \text{V}$, rather than leaving it at $\pm 15\ \text{V}$. Adjusting the power supply keeps the op amp's input voltage relative to the power-supply rails, which minimizes errors caused by common-mode voltages at the op amp's output.

Can you simply add an op amp to your four-wire DMM to obtain the six-wire guarding capability?

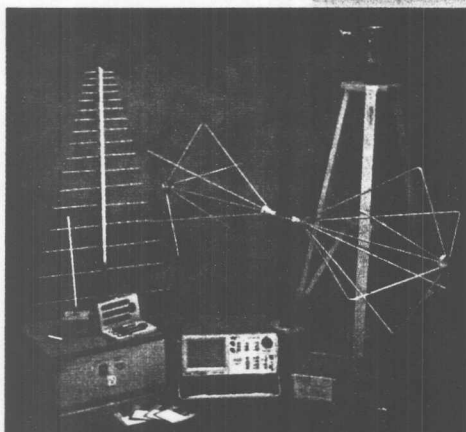You can, but you must know how much measurement error you can tolerate. According to Chuck Cimino at Keithley Instruments, you should take a system approach to adding your own guard circuit. Your approach will depend on the resistance range you want to measure, which also affects the amount of I_{test} you



Preamplifiers
Spectrum Analyzers
Near Field Probes
Antennas
Antenna Masts & Tripods
Turntables
Signal Generators
Comb Generators
LISNs
Safety (UL/CSA)
Telecom (FCC, CS03)

EMC Test Solutions

In-house EMC testing is now affordable! Com-Power's **NEW** PC-113 EMI emissions system, available for under \$9000, can save you time and money by allowing you to do EMC testing at your facility. The system includes:

- Digital spectrum analyzer (150 kHz to 1050 MHz)
- Near field probes (E & H field probes)
- Calibrated antennas (30 to 1000 MHz) and antenna tripod
- High gain preamplifier (32 db, 1 to 1000 MHz)
- Line impedance stabilization network (150 kHz to 30 MHz)
- Comb generator (1 to 1000 MHz, 1 or 5 MHz step)
- Automated measurement software

Call for EMI Test Equipment catalog (949) 587-9800

or visit us at
www.com-power.com



Competitive pricing

Fast delivery

Two year warranty

20621 Pascal Way • Lake Forest, CA 92630 • (949) 587-9800 • fax (949) 587-9960 • sales@com-power.com

current that the op amp must supply.

You'll need an op amp with a high input impedance, typically in the gigohms range. To minimize errors, you also should look for an op amp with the lowest possible input bias current. Remember, any current that flows into the op amp will change the value of I_{test} . The

into greater errors for a given amount of bias current.

You'll also need to minimize V_{OS} , which you can do with a potentiometer connected to the op amp's offset-compensation pins (not shown in Fig. 2). Using a manual offset adjustment is fine for lab work. For production, where you

the offset compensation frequently, perhaps every day depending on the accuracy you need. An op amp's V_{OS} can slowly drift because the device self-heats, particularly as the guard current G_{source} nears the op amp's maximum current output. According to Tee Sheffer, president of Signametrics (Seattle, WA), the greater an op amp's output current, the greater its V_{OS} , so you may trade one error source for another.

Choose an op amp with as high a common-mode rejection ratio (CMRR) as possible. Otherwise, the op amp's CMRR will contribute an error that may exceed the error caused by V_{OS} .

You may not find an op amp that has the spec for every characteristic that affects your measurements. Still, by calculating the amount of error you can tolerate, you can select an op amp that adequately meets your needs.

If you need to measure in-circuit resistors in production or incoming inspection, you can add switches to your test setup to measure various resistances or those in several circuits at once. But you must account for additional errors from the switches and cables. According to Sheffer, thermal EMF voltages across the switches can add significant errors depending on the resistor values in your device under test.

You may also need several feet of cable between your DMM and devices under test. In these situations, IR voltages in the cables and thermal EMF voltages—as high as 300 μV —across the switches can introduce measurement errors. To minimize these errors, connect G_{sense} and G_{source} as close to the DUT as possible. If you're making measurements in the lab with short cables and no switches, then you can connect G_{sense} to G_{source} at the meter. Use copper wire to minimize thermocouple EMFs caused by the junction of dissimilar metals.

T&MW

FOOTNOTE

1. Schwertner, Thomas, *Obtaining More Accurate Resistance Measurements Using the 6-Wire Ohms Technique*, Keithley Instruments, Cleveland, OH, www.keithley.com/white_papers/schwertner/sixohms.html.

You can contact Martin Rowe at mrowe@cahners.com

AMREL

QUALITY POWER SUPPLIES

Advanced Line of Linear Programmable DC Power Supplies

THE PD SERIES PROVIDES

- Widest Selection
- Unlimited Combinations
- "One-Box" Interface Design
- Custom Design and Modifications

KEY FEATURES

- Co-existent GPIB and RS-232 Standard Interface
- Close-Case Calibration
- Master / Slave Capability
- Multiple Power Levels from 20 - 1,200 watts
- Low Ripple and Noise (PARD) Output
- Dynamic Power Profile Programming Capability (99-points)
- Power Off Memory
- CE-Mark Compliance

AMERICAN RELIANCE, INC.

11801 Goldring Road • Arcadia, CA 91006
TOLL FREE: (800) 654-9838 • Fax: (626) 358-3838
www.amrel.com